

CSE 232 Spring 2021 Homework 4	
Student Name: Aygün Bayır	Student ID: 161044119

### Step 1: Define MUX size

Register will have following operations:

- Clear
- Load
- Swap


Hence there are 3 operations I am going to use

4x1 multiplexer

### Step 2: Create MUX operation table

s1	s0	Operation
0	0	Maintain present value
0	1	Clear (cl)
1	0	Load (ld)
1	1	Swap (sw)

### Step 3 : Connect MUX inputs

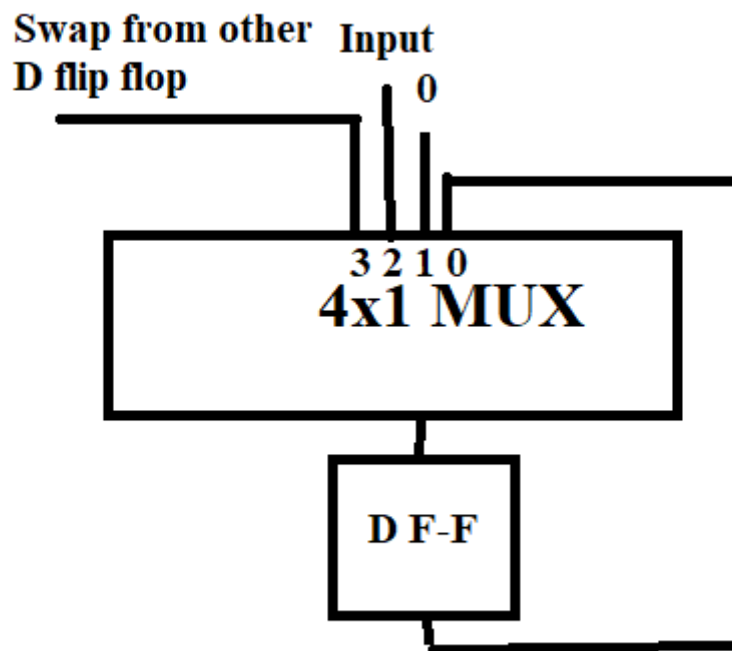

#### Step 4: Map control lines

The priority rank is clear, load, swap


Inputs			Outputs		
cl	ld	sw	s1	s0	Operation
1	x	X	0	0	Maintain present value
1	x	X	0	1	Clear
0	1	x	1	0	Load
0	0	1	1	1	Swap

$$s1 = cl' * ld + cl' * ld' * sw$$

$$s0 = cl + cl' * ld' * sw$$

#### Step 5: Drawing Circuits

Combinational Circuit

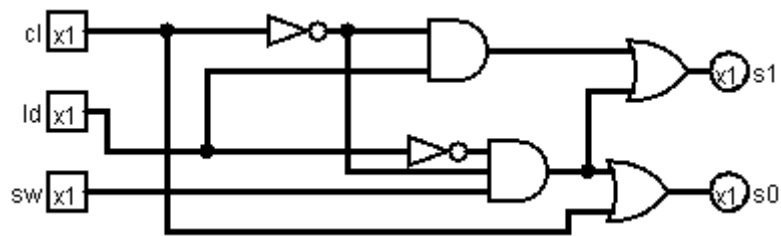

Register on the next page

